

CMPE 314 Midterm Exam-1 Solutions

Spring
2018

P1

(a) For p-region

Dopant type: acceptor, group III atoms


Dopant concentration: $N_A = p_0 = 8 \times 10^{14} \frac{1}{\text{cm}^3}$

For n-region

Dopant type: donor, group V atoms

Dopant concentration: $N_D = n_0 = 2 \times 10^{15} \frac{1}{\text{cm}^3}$

(b)

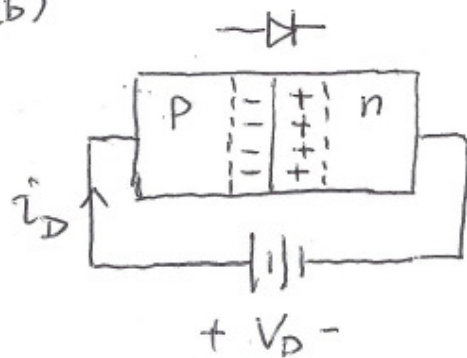

potential
barrier

• Forward bias $V_D > 0$

potential barrier decreases

electrons moving from n-region to p-region

holes moving from p-region to n-region

diffusion current

• Reverse bias $V_D < 0$

potential barrier increases

holes moving from n-region to p-region

electrons moving from p-region to n-region

drift current

P2

$$\left. \begin{array}{ll} \text{KCL} & I_I = I_{D1} + I_{D2} \\ \text{KVL} & V_{D1} = V_{D2} + R I_{D2} + V^- \\ \text{diode-1} & I_{D1} = I_{S1} (e^{V_{D1}/V_T} - 1) \\ \text{diode-2} & I_{D2} = I_{S2} (e^{V_{D2}/V_T} - 1) \end{array} \right\} \begin{array}{l} 4 \text{ equations} \\ \text{for 4 unknowns} \\ (I_{D1}, I_{D2}, V_{D1}, V_{D2}) \end{array}$$

Since diode full models are used, there are no requirements on minimum V^+ , V^- , I_I .

P3

① $V_s > V_{x3} + V_{x4}$, $D3$ and $D4$ on, $D1$ and $D2$ off

$$V_o(t) = -[V_s(t) - V_{x3} - V_{x4}] = -V_s(t) + 2V_f$$


$$V_o(\text{peak}) = -10 + 1.4 = -8.6 \text{ V}$$

② $V_s < -(V_{x1} + V_{x2})$, $D1$ and $D2$ on, $D3$ and $D4$ off

$$V_o(t) = -[-V_s(t) - V_{x1} - V_{x2}] = V_s(t) + 2V_f$$

$$V_o(\text{peak}) = -10 + 1.4 = -8.6 \text{ V}$$
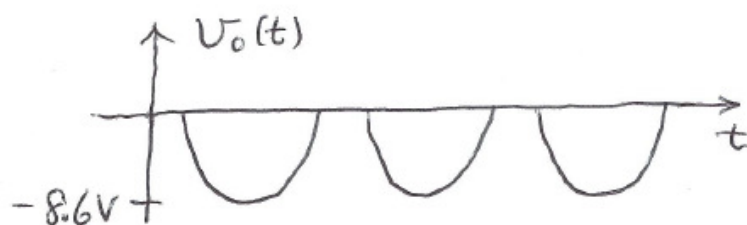
$$\text{PIN} > V_s(\text{peak}) - V_f = 9.3 \text{ V}$$



P4

(a) (1) $V_I > V_{D1} + V_{Z1}$, D_1 on, D_2 reverse break down, D_2 off

$$V_o(t) = V_{D1} + V_{Z1}$$

(2) $V_I < -(V_{D2} + V_{Z2})$, D_2 on, D_1 reverse break down, D_1 off

$$V_o(t) = -(V_{D2} + V_{Z2})$$


(3) $-(V_{D2} + V_{Z2}) < V_I < V_{D1} + V_{Z1}$, D_1 and D_2 off

$$V_o(t) = V_I(t)$$

(b)

$$V_o(\max) = V_{D1} + V_{Z1} = 0.7 + 10 = 10.7 \text{ V}$$
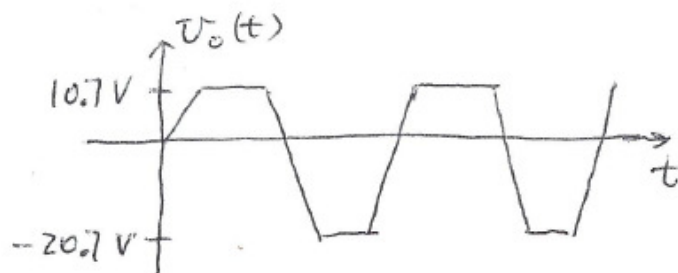
$$V_o(\min) = -(V_{D2} + V_{Z2}) = -(0.7 + 20) = -20.7 \text{ V}$$




It is a double clipper circuit.

P5

(a) Let $v_C(0) = 0$

$$v_D = v_I - (-V_B) = v_I + V_B$$

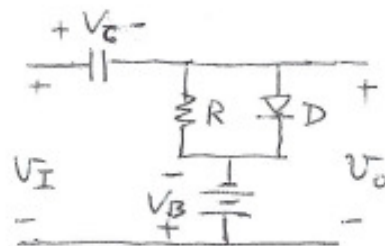

When $v_I(t) + V_B > V_f$, diode on, capacitor charging

$$v_C(t) = v_I(t) - (V_f - V_B)$$

$$v_C(\max) = v_I(\max) - V_f + V_B$$

When $v_I(t) < v_I(\max)$, diode off, capacitor discharging very slowly.

$$v_C \approx v_C(\max)$$

In the steady state

$$v_O(t) = v_I(t) - v_C$$

$$= v_I(t) - v_I(\max) + V_f - V_B$$

Diode voltage


$$v_D(t) = v_O(t) - (-V_B)$$

$$= v_I(t) - v_I(\max) + V_f < V_f \quad \text{diode is off.}$$

(b) $v_C(\max) = v_I(\max) - V_f + V_B$

$$= 30 - 0.7 + 5 = 34.3 \text{ V}$$

$$v_O(t) = v_I(t) - 34.3 \text{ V}$$

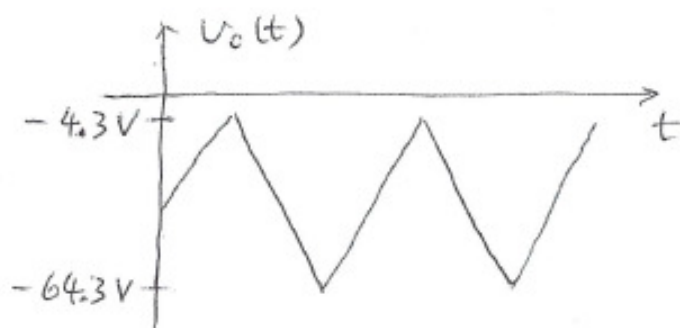

It is a clamper circuit.

P6

$V_Z = -5\text{ V}$, diode is in forward bias.

$$V_D = V_Z + r_f I_D$$

$$\frac{V_L - V_Z}{R_i} + \frac{V_L - (-V_Z)}{r_f} + \frac{V_L}{R_L} = 0$$

$$\frac{V_L + 5}{100} + \frac{V_L + 0.7}{5} + \frac{V_L}{200} = 0$$

$$\rightarrow V_L = -0.884\text{ V} = -V_D$$

$$I_D = \frac{V_D - V_Z}{r_f} = \frac{0.884 - 0.7}{5} = 0.037\text{ A}$$

$$P_D = V_D I_D = 0.033\text{ W}$$

