

Nem Negash

CMPE 415

Prof. Tinoosh Mohsenin

April 18, 2021

## HW5 Report

### Problem 1:

The adder timing results:

```
create_clock -period 2.155 -name clk -waveform {0.000 1.0775} -add [get_ports clk]
```


Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 0.163 ns	Worst Hold Slack (WHS): 0.190 ns	Worst Pulse Width Slack (WPWS): 0.000 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 11	Total Number of Endpoints: 11	Total Number of Endpoints: 33

All user specified timing constraints are met.

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.


**Total On-Chip Power:** 0.128 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 25.6°C  
**Thermal Margin:** 59.4°C (12.9 W)  
**Effective  $\theta_{JA}$ :** 4.6°C/W  
**Power supplied to off-chip devices:** 0 W  
**Confidence level:** Low

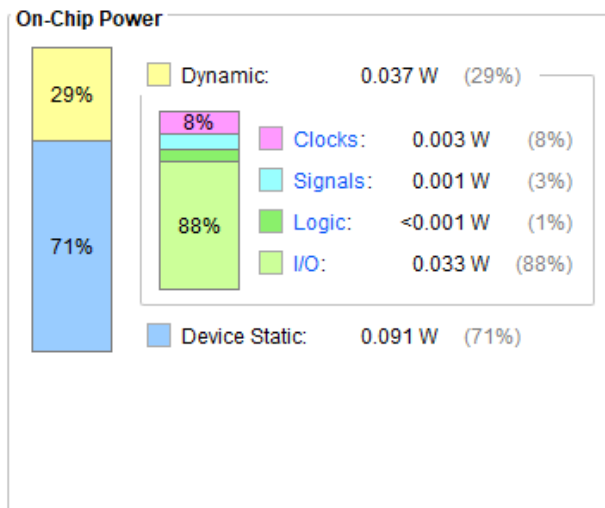[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



I couldn't have the negative slack be less than 0.15 because when I had it below my width slack goes into negative.

The schematic:

 

The multiplier timing results:

```
create_clock -period 12 -name clk -waveform {0.000 6} -add [get_ports clk]
```

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 0.017 ns	Worst Hold Slack (WHS): 0.341 ns	Worst Pulse Width Slack (WPWS): 5.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 40	Total Number of Endpoints: 40	Total Number of Endpoints: 81


All user specified timing constraints are met.

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** 0.128 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 25.6°C  
**Thermal Margin:** 59.4°C (12.9 W)  
**Effective  $\theta_{JA}$ :** 4.6°C/W  
**Power supplied to off-chip devices:** 0 W  
**Confidence level:** Low


[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

#### On-Chip Power

 


I was able to have the negative slack be less than 0.15.

The schematic:

 

Problem 2:

**Design**

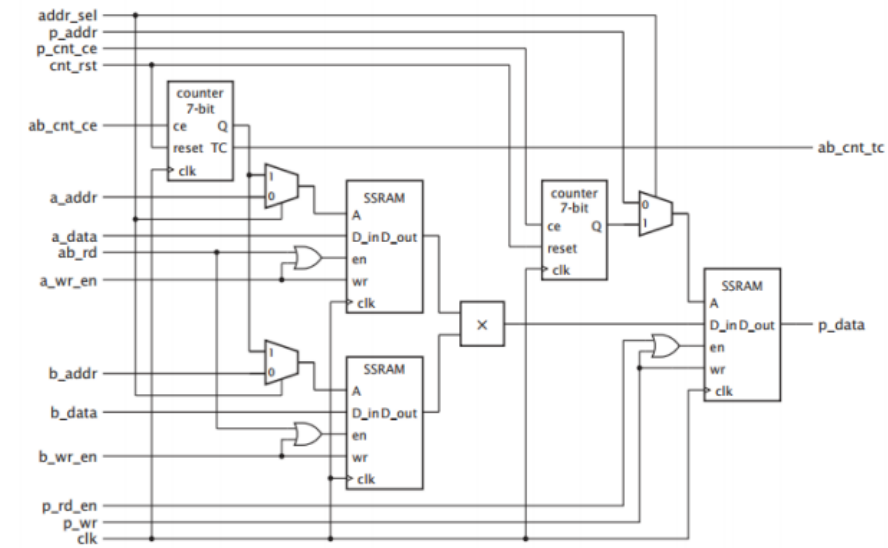

state	start	Ab_cn_tc	next	Cnt_rst	Ab_cnt_ce Ab_rd	P_cnt_ce P_wr	done
idle	0	-	idle	1	0	0	0
idle	1	-	Cmp0	0	1	0	0
cmp0	-	-	comp	0	1	1	0
comp	-	0	comp	0	1	1	0
comp	-	1	last	0	1	1	0
last	-	-	Result	0	0	1	0
result	-	-	idle	1	0	0	1

## Behavioral Simulations

i. testbench

```

module tb_part2;
//inputs
reg clk,rst, start, a_write_en, b_write_en, p_read_en;
reg [6:0] a_addr, b_addr, p_addr;
reg signed [15:0] a_data, b_data;
integer count = 0;
//fucntion instantiation
part2 test(.clk(clk), .rst(rst), .start(start), .a_write_en(a_write_en), .b_write_en(b_write_en), .p_read_en(p_read_en),
.a_addr(a_addr), .b_addr(b_addr), .p_addr(p_addr),
.a_data(a_data), .b_data(b_data),
.p_data(p_data),
.done(done));

//clk set up
always#1 clk = !clk;
initial begin
clk = 0;
//reset
rst = 1;
#10
rst = 0;
#5
//Initialize Inputs
start = 1;
a_write_en = 1;
b_write_en = 1;
p_read_en = 1;
a_addr = 0;
b_addr = 0;
p_addr = 0;
a_data = 1;
b_data = 127;
while(count < 128)begin //change input values
#10
a_addr = a_addr + 1;
b_addr = b_addr + 1;
p_addr = p_addr + 1;
a_data = a_data + 1;
b_data = b_data - 1;
count = count + 1;
end
end
endmodule

```

## Implementation Results

```
create_clock -period 2.4 -name clk -waveform {0.000 1.2} -add [get_ports clk]
```

Setup		Hold		Pulse Width	
Worst Negative Slack (WNS):	0.022 ns	Worst Hold Slack (WHS):	0.212 ns	Worst Pulse Width Slack (WPWS):	0.245 ns
Total Negative Slack (TNS):	0.000 ns	Total Hold Slack (THS):	0.000 ns	Total Pulse Width Negative Slack (TPWS):	0.000 ns
Number of Failing Endpoints:	0	Number of Failing Endpoints:	0	Number of Failing Endpoints:	0
Total Number of Endpoints:	21	Total Number of Endpoints:	21	Total Number of Endpoints:	11

All user specified timing constraints are met.


### On-Chip Power

The diagram shows a total power consumption of 0.087 W (97%). It is broken down into two main categories: Device Static (0.084 W, 97%) and Dynamic (0.003 W, 3%). The Dynamic power is further broken down into Clocks (0.002 W, 80%), Signals (<0.001 W, 4%), Logic (<0.001 W, 4%), and I/O (<0.001 W, 12%).

Category	Power (W)	Percentage
Device Static	0.084 W	97%
Dynamic	0.003 W	3%
Clocks	0.002 W	80%
Signals	<0.001 W	4%
Logic	<0.001 W	4%
I/O	<0.001 W	12%

Name	Slice LUTs (63400)	Slice Registers (126800)	Slice (15850)	LUT as Logic (63400)	Bonded IOB (210)	BUFGCTRL (32)
N part2	14	13	5	14	36	1

## Design

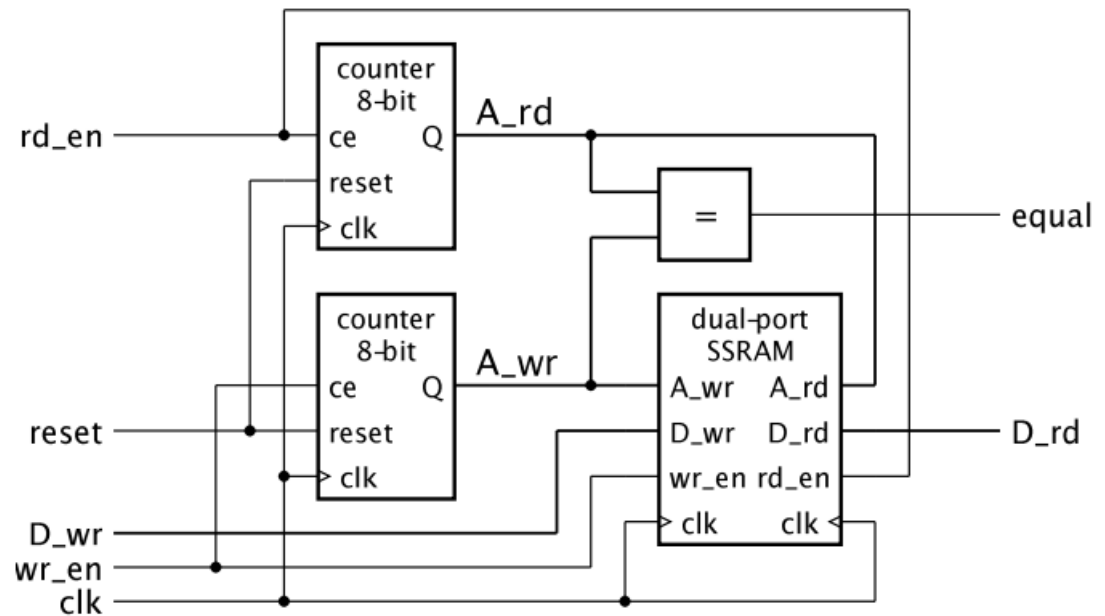

## Behavioral Simulations

- i. testbench

```

module tb_part3;

reg clk;
reg reset;
reg rd_en;
reg wr_en;
reg [15:0] data_in;

wire full;
wire empty;
wire [15:0] data_out;
integer i, fid_in, fid_out, status;
part3 uut (.clk(clk), .reset(reset), .rd_en(rd_en), .wr_en(wr_en), .full(full), .empty(empty), .data_in(data_in), .data_out(data_out));
always # 10 clk = ~ clk;

initial begin
// Initialize Inputs
clk = 0;
reset = 0;
rd_en = 0;
wr_en = 0;
data_in = 0;

#40;
reset =1;
#90;
reset =0;

for(i=1;i<257;i=i+1)
begin
wr_en=0;
data_in = i;
wr_en=1;
#20;
end
wr_en=0;
#40;
rd_en =1;
#500;
end

endmodule

```

### Implementation Results [5pts]

```
create_clock -period 3.5 -name clk -waveform {0.000 1.75} -add [get_ports clk]
```


Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 0.021 ns	Worst Hold Slack (WHS): 0.234 ns	Worst Pulse Width Slack (WPWS): 0.556 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 52	Total Number of Endpoints: 52	Total Number of Endpoints: 21

All user specified timing constraints are met.

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** 0.115 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 25.5°C  
 Thermal Margin: 59.5°C (12.9 W)  
 Effective  $\theta_{JA}$ : 4.6°C/W  
 Power supplied to off-chip devices: 0 W  
 Confidence level: Low

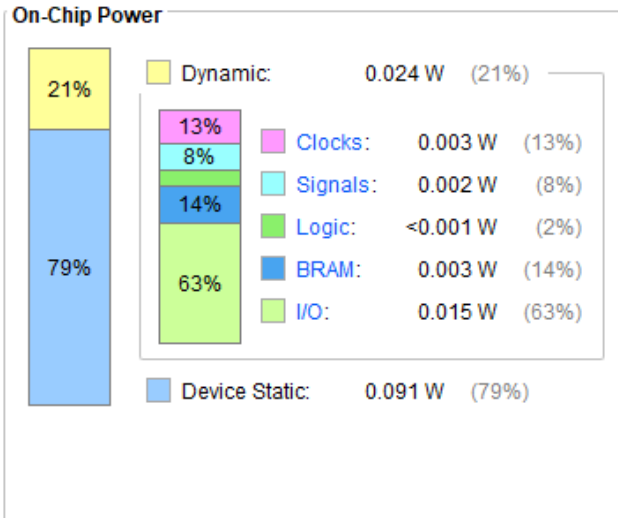[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



Name ^ 1	Slice LUTs (63400)	Slice Registers (126800)	Slice (15850)	LUT as Logic (63400)	Block RAM Tile (135)	Bonded IOB (210)	BUFGCTRL (32)
N part3	39	18	24	39	0.5	150	1