

P1


(a) Dopant type: acceptor, group III atoms

Dopant concentration  $N_a = p_o = 8 \times 10^{14} \frac{1}{\text{cm}^3}$ 

Minority carrier is electron.

Electron concentration  $n_o = \frac{n_i^2}{p_o} = \frac{n_i^2}{N_a}$ 

(b)

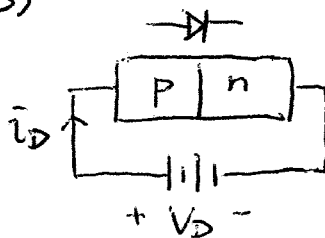

Forward bias: majority carriers

electrons moving from n-region to p-region.

holes moving from p-region to n-region

Reverse bias: minority carriers

holes moving from n-region to p-region

electrons moving from p-region to n-region

Reverse break down: excess carriers

electrons and holes generated in the space-charge region. Holes moving to p-region, electrons moving to n-region

P2

$$(a) \quad I_I = I_{R_1} + I_D$$

$$I_{R_1} = \frac{V_c}{R_1}$$

$$I_D = I_s (e^{V_D/V_T} - 1)$$

$$V_o = V_B + V_D$$

(b) ① When  $I_I$  is too small,  $I_D = 0$ , diode is off

$$V_o = R_1 I_I \leq V_B + V_g$$

② When  $R_1 I_I > V_B + V_g$ , diode is on

$$I_I = I_{R_1} + I_D$$

$$I_{R_1} = \frac{V_o}{R_1}$$

$$V_D = V_g + r_f I_D$$

$$V_o = V_B + V_D$$


P3

When  $U_s > V_g \rightarrow D_1 \text{ off} \rightarrow U_o = -U_s + V_g$   
 $D_2 \text{ on}$

$$U_{o, \max} = -5 + 0.7 = -4.3V$$

When  $U_s < -V_g \rightarrow D_1 \text{ on} \rightarrow U_o = U_s + V_g$   
 $D_2 \text{ off}$

$$U_{o, \max} = -5 + 0.7 = -4.3V$$

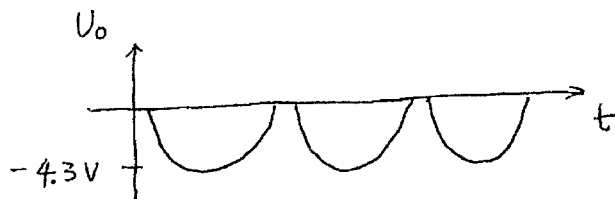

negative full-wave  
rectifier

P4

(a)  $V_I < V_B - V_f$ , diode on


$$V_o = V_B - V_f$$

$V_I > V_B - V_f$ , diode off

$$V_o(t) = V_I(t)$$

(b)  $V_B - V_f = 5 - 0.7 = 4.3V$

clipper circuit

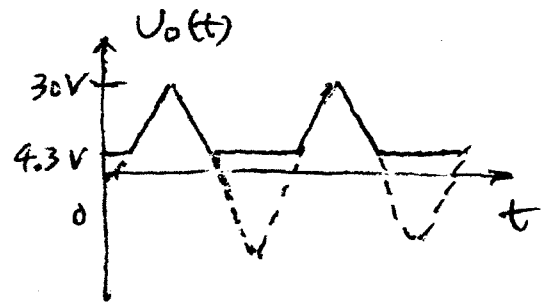

P5

(a) Let  $V_c(0) = 0$

When  $V_I > V_B + V_f$ , diode on, capacitor charging

$$V_c(t) = V_I(t) - (V_B + V_f)$$

$$V_c(\max) = V_I(\max) - (V_B + V_f)$$

When  $V_I < V_B + V_f$ , diode off  
capacitor discharging slowly

$$V_c \approx V_c(\max)$$

In steady state



$$V_o(t) = V_I(t) - V_c(\max)$$

$$V_o(t) = V_o(t) - V_B = V_I(t) - V_I(\max) + V_f < V_f, \text{ diode off.}$$

(b)  $V_c(\max) = 30 - (2 + 0.7)$   
 $= 27.3V$

$$V_c(t) = V_I(t) - 27.3V$$

clamper circuit

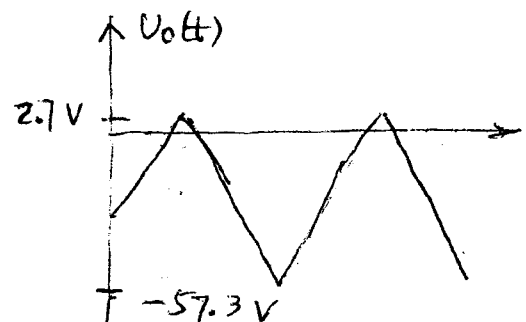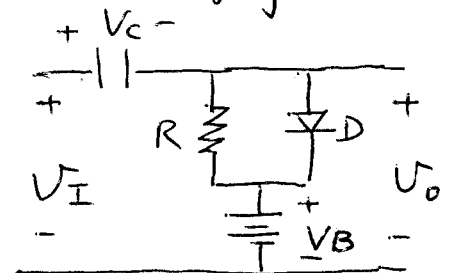

P6

(a)  $V_{ps} > V_{z0}$

Zener diode is reverse break down

$$V_z = V_{z0} + r_z I_z$$


$$\frac{V_o - V_{ps}}{R} + \frac{V_o - V_{z0}}{r_z} + \frac{V_o}{R_L} = 0$$

$$V_o \left( \frac{1}{R} + \frac{1}{r_z} + \frac{1}{R_L} \right) = \frac{V_{ps}}{R} + \frac{V_{z0}}{r_z}$$

$$\rightarrow V_o = V_z = 5.073 \text{ V}$$

$$I_z = \frac{V_z - V_{z0}}{r_z} = \frac{5.073 - 5}{10} = 7.3 \text{ mA}$$
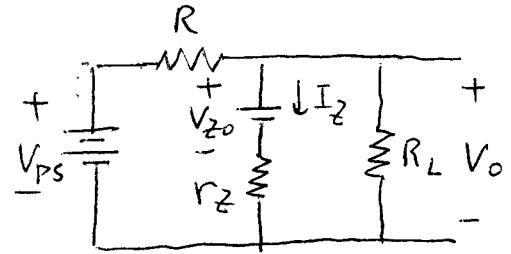
$$P_z = V_z I_z = (5.073 \text{ V}) \times (7.3 \text{ mA}) = 3.7 \text{ mW}$$



$$V_{ps} = 10 \text{ V}$$

$$R = 500 \Omega$$

$$R_L = 2 \text{ k}\Omega$$

$$V_{z0} = 5 \text{ V}, r_z = 10 \Omega$$

(b)  $R_L = \infty$

$$\frac{V_o - V_{ps}}{R} + \frac{V_o - V_{z0}}{r_z} = 0$$

$$V_o \left( \frac{1}{R} + \frac{1}{r_z} \right) = \frac{V_{ps}}{R} + \frac{V_{z0}}{r_z}$$

Variation of  $V_o$  due to variation of  $V_{ps}$

$$\Delta V_o \left( \frac{1}{R} + \frac{1}{r_z} \right) = \frac{\Delta V_{ps}}{R}$$

$$\rightarrow \frac{\Delta V_o}{\Delta V_{ps}} = \frac{r_z}{R + r_z} = \frac{10}{500 + 10} = 1.96\%$$