

Nem Negash

CMPE 415

Prof. Mohsenin

February 21th 2021

Homework 1 Report

Statement of Project Completion

What I got to work:

Problem 1:

- a) Implemented truth table as shown in the wave form.

```
`timescale 1ns / 1ps

module part1();

    //inputs

    reg a = 1'b0;

    reg b = 1'b0;

    reg c = 1'b0;

    //outputs

    reg out_reg = 1'b0;

    always @(*)

    begin
```

```

        case ({c,b,a})//case statment using the inputs

            3'b000 : out_reg = 1;

            3'b001 : out_reg = 1;

            3'b100 : out_reg = 0;

            3'b101 : out_reg = 0;

            3'b110 : out_reg = 1;

            3'b111 : out_reg = 0;

        endcase

    end

//testbench

initial begin

    //forloop that checks using all forms of inputs

    for(reg[2:0] temp = 3'b000; temp < 8; temp = temp + 1)

    begin

        a = temp[0];

        b = temp[1];

        c = temp[2];


        #50;

    end

end


endmodule

```

 

The waveform shows the exact truth tables with the 'don't care' values as ones.

b) Completed the RTL Schematic.

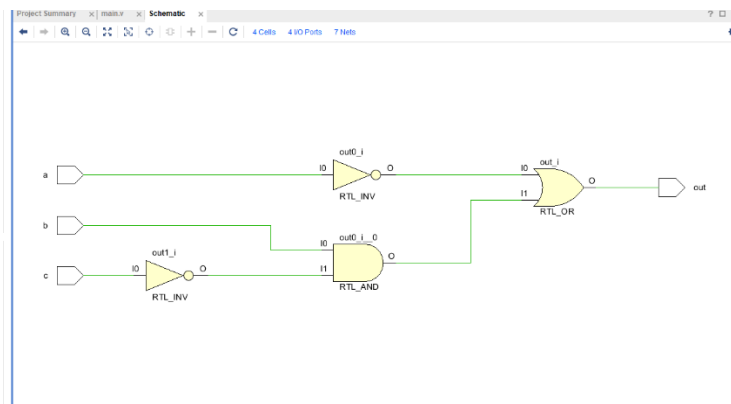

Problem 2:

a) Designed and implemented each ALU operations

``timescale 1ns / 1ps`

`module part2(`

`input signed [8:0] A,B, // inputs`

`input signed [3:0] S, // select`

`output signed [8:0] Q // output`

`);`

`reg signed [8:0] Result;`

`assign Q = Result; // out`

```

reg [8:0] count = 9'b000000000;//counter for rotate

always @(*)

begin

    case(S)

        4'b0000: begin // Addition0

            Result = A + B ;

        end

        4'b0001: begin // Subtraction1

            Result = A - B ;

        end

        4'b0010: begin// Multiplication2

            Result = A * B;

        end

        4'b0011: begin// Logical shift right3

            Result = B>>A;

        end

        4'b0100: begin// Rotate left4

            Result = {B[9:0]};

            for(count = 0; count < A; count = count + 1'b1)

                begin

                    Result = {Result[7:0],Result[8]};

                end

            end

        end

```

```

4'b0101: begin// Logical or 5
    Result = A | B;

end

4'b0110: begin// Logical and 6
    Result = A & B;

end

4'b0111: begin// Logical nand 7
    Result = !(A & B);

end

4'b1000: begin// Logical xnor 8
    Result = 9'b11111111 ^ (A ^ B);

end

4'b1001: begin// complement of B 9
    Result = (B ^ 9'b11111111) + 1'b1;

end

default: Result = 9'b000000000 ;

endcase

end

endmodule

```

b) Conducted a test bench for each operation with all possible edge cases.

```
`timescale 1ns / 1ps
```

```

module tb_part2;

reg[8:0] A,B;

reg[3:0] S;


//Output

wire[8:0] Q;

//counter

reg[3:0] i;

part2 test_unit(
    .A(A),.B(B), //Inputs
    .S(S),//Select
    .Q(Q)//output
);

initial begin

// testing all 0s

A = 9'b000000000;

B = 9'b000000000;

S = 4'b0000

#15

for (i=0;i <= 9;i = i+ 1'b1)

begin

S = S + 4'b0001;

#15;

```

```

end

//testing all 1s

A = 9'b0000000001;

B = 9'b0000000001;

S = 4'b0000;

#15

for (i=0;i <= 9;i = i+ 1'b1)

begin

    S = S + 4'b0001;

    #15;

end;

//testing all positive inputs

A = 9'b000101001;

B = 9'b000100001;

S = 4'b0000;

#15

for (i=0;i <= 9;i = i+ 1'b1)

begin

    S = S + 4'b0001;

    #15;

end;

//testing all negative inputs

A = 9'b111101111;

```

```

    B = 9'b111101101;

    S = 4'b0000;

    #15

    for (i=0;i <= 9;i = i+ 1'b1)

    begin

        S = S + 4'b0001;

        #15;

    end;

    //testing one positive and one negative input

    A = 9'b101100001;

    B = 9'b000100001;

    S = 4'b0000;

    #15

    for (i=0;i <= 9;i = i+ 1'b1)

    begin

        S = S + 4'b0001;

        #15;

    end;

    A = 9'b000000000;



    B = 9'b000000000;

    S = 4'b0000;

end

endmodule

```

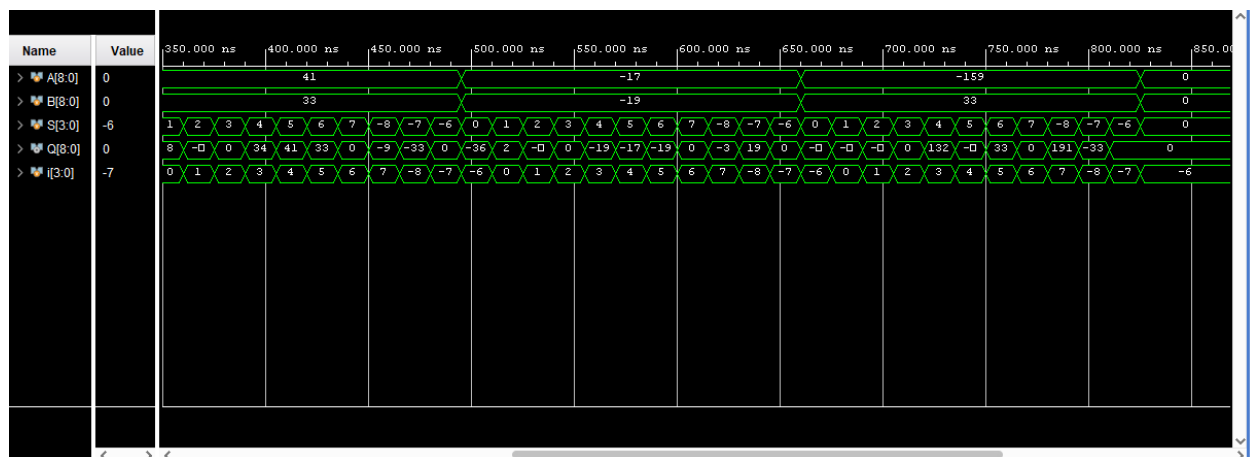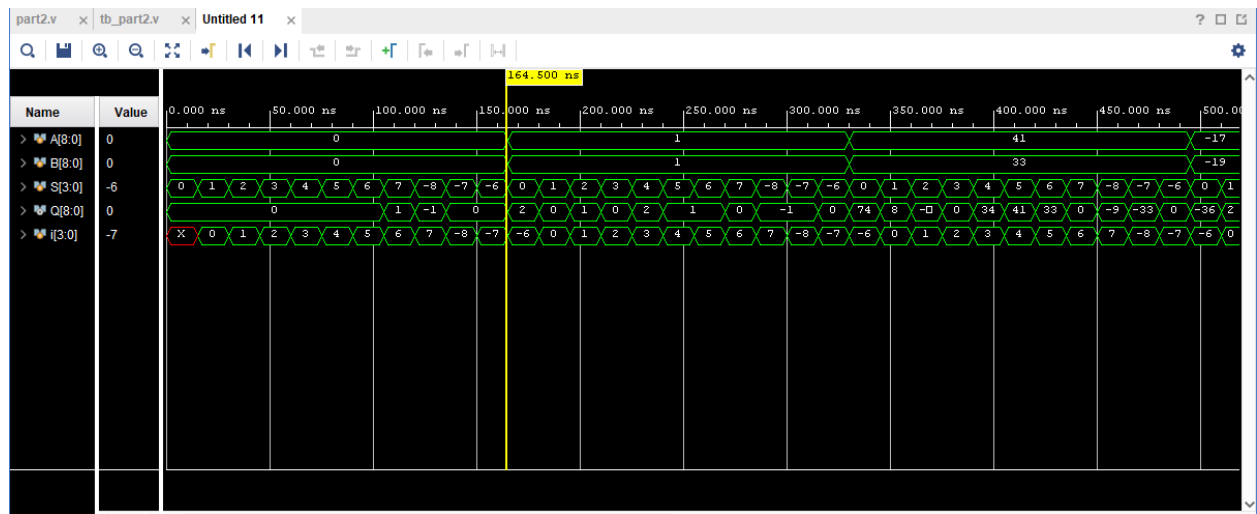The waveform diagram shows the input values with all edge cases and their output for each operation.

Problem 3:

This part was not completed (Look at the “What I did not get to work” section).

Problem 4:

a) Implement Verilog code to represent a 4-bit counter.

timescale 1ns / 1ps

module part4(input CLK, CLR,ENABLE, UP,LOAD, //single bit inputs

```

    output reg [3:0] Q, //output

    input [3:0] V, //load value

    output reg RC0); //single bit output

//at clock edge

always @(posedge CLK )

begin

    RC0 = 1'b0; //start with RC0 as 0

    if (CLR) //if clear is 1

        Q = 4'b0000;

    else //if clear is 0

        if(ENABLE)

            if(LOAD) //is load is 1

                Q = V;

            else //if load is 0

                if (UP) //if up is 1

                    Q = Q + 1'b1;

                if(!UP) //if up is 0

                    Q = Q - 1'b1;

                if(Q == 4'b1111 | Q == 4'b0000) //if the output is 15 or 0

                    RC0 = 1'b1;

        end

    endmodule

```

- b) Create a test bench for the test bench as specified in the project description

```

`timescale 1ns / 1ps

module tb_part4;

//variables

reg clk,clr,enable,up,load;

reg[3:0] V;

wire [3:0] Q;

wire rc0;


part4 test_unit(.CLK(clk),.CLR(clr), .UP(up), .Q(Q), .ENABLE(enable),
.LOAD(load), .V(V), .RC0(rc0));

//start clock

always #5 clk = (clk ^ 1'b1);


initial begin

//setup

clk = 0;

#5

up = 1;

#10

clr = 1;


//first 10 cycles

#10

```

```
clr = 0;

enable = 1;

up = 1;

load = 0;

//hold value for 5 cycles

#100 enable = 0;

//count down for 20 cycles

#50 enable = 1; up = 0;

//clear counter

#195 clr = 1;

//load V value into counter

#5 clr = 0; V = 4'b1100; load = 1; up = 1;

#5 clr = 0; load = 0;




//count up for 11 cycles

#115 enable = 0;

end

endmodule
```

c) Verify code with wave form diagram

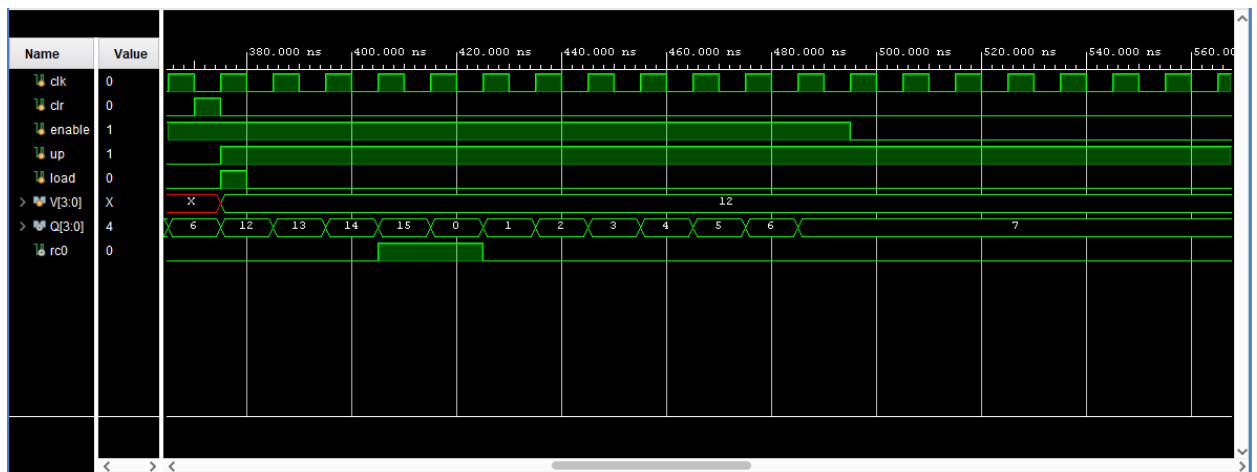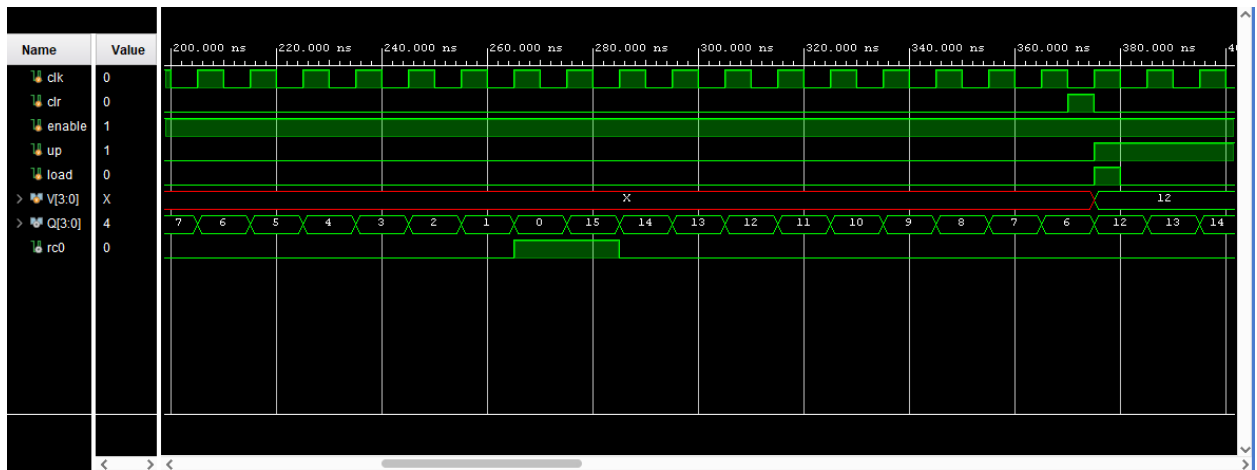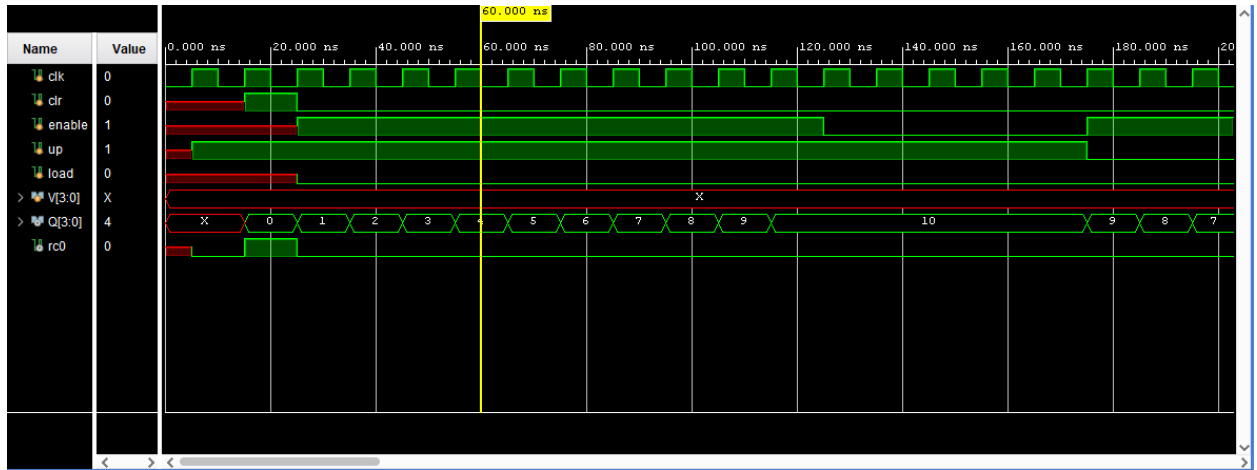

What I did not get to work:

Problem 1:

- a) I was not able to have a separate test bench file as a simulation source. My test bench is written within the design file

Problem 2:

- a) I wasn't able to have each operation within its own module but rather all in one file.

Problem 3:

- a) I wasn't able to figure out how to have the output be a registered output without just assigning the output to a reg variable.

Problem 4:

- a) Completed with no exceptions.