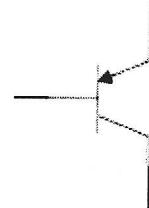


## CMPE 314 Midterm Exam 2

(November 10, 2016)


### Problem 1 (10 points)

For the transistor shown, draw the internal structure and show power supply connections and conditions on polarity and magnitude in the forward-active mode. Describe actions of carriers (specify types and directions) in different regions.



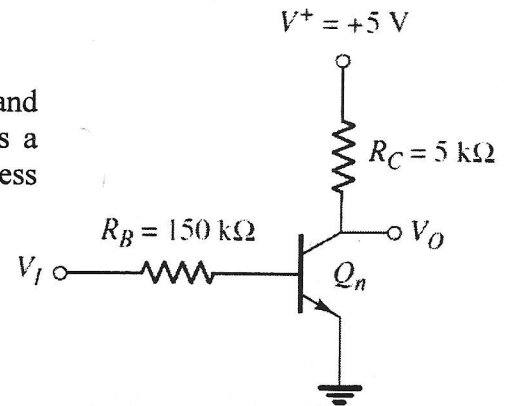
### Problem 2 (15 points)

Assume the transistor has its properties  $\beta$ ,  $V_{BE(on)}$ , and  $V_{CE(sat)}$ , and  $V^+$  is fixed. Determine the output  $V_O$  as a function of the input  $V_I$  for a large range of  $V_I$ . Express results in terms of symbols.


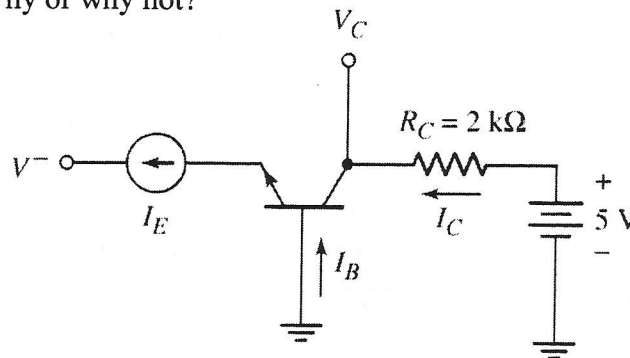
### Problem 3 (20 points) *values*

For the transistor shown in the circuit,  $\beta=80$ ,  $V_{BE(on)}=0.7$  V,  $V_{CE(sat)}=0.2$  V. Let  $I_E=1.2$  mA. Determine the power dissipated by the transistor. Is the transistor in the forward-active mode? Why or why not?



### Problem 4 (25 points)

- Find the DC load-line.
- Assume finite  $V_A$ . Draw the small-signal circuit with the transistor hybrid- $\pi$  model.
- Find the AC load-line. Plot the Q-point, DC loadline and AC loadline (indicate loadline slopes) in the  $i_C$  vs  $v_{CE}$  diagram.
- Find the maximum and minimum possible values of  $v_{CE}$  without distortion for small-signal amplification. (Work with symbols for Problem 4)